

PHY-112


PRINCIPLES OF PHYSICS-II

AKIFUL ISLAM (AZW)

SPRING-24 | CLASS-16

COMBINATIONS OF RESISTORS: SERIES

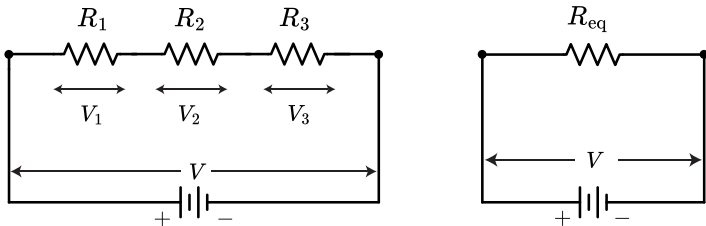
The voltage across each resistor **is not** the same. The total voltage across the series combination equals the sum of the voltages across each resistor.



$$R_{eq} = R_1 + R_2 + R_3 = \sum_i^n R_i$$

COMBINATIONS OF RESISTORS: PARALLEL

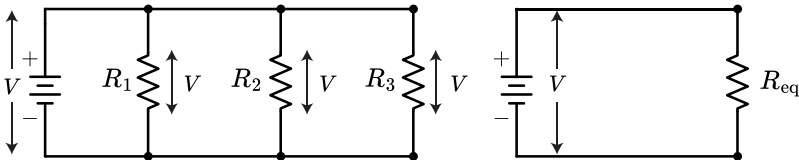The voltage across each resistor **is** the same. The total current through the parallel combination is the sum of the currents through each individual resistor.




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \sum_i^n \frac{1}{R_i}$$

KIRCHHOFF'S TWO RULES FOR CIRCUITS

KIRCHHOFF'S 1ST RULE: CURRENT RULE OR JUNCTION RULE

Because **electric charge is conserved**, the total current into the junction must equal the total current leaving the junction. That is,

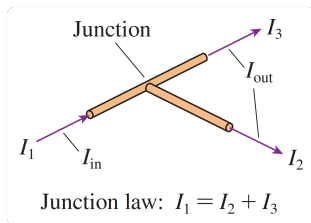
$$\sum I_{\text{in}} = \sum I_{\text{out}}$$



KIRCHHOFF'S 2ND RULE: VOLTAGE RULE OR LOOP RULE

Because **energy is conserved**, a charge that moves around a closed path has $\Delta U_{\text{elec}} = 0$. In a circuit, the algebraic sum of all potential differences sum to zero.
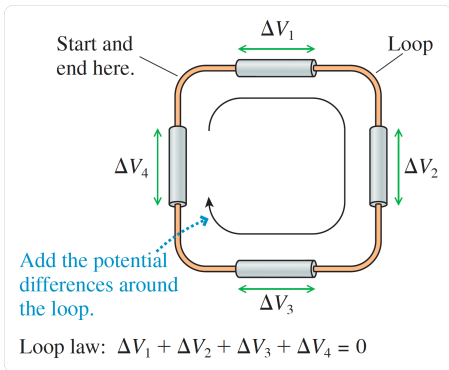
$$\Delta V_{\text{loop}} = \sum_i (\Delta V)_i = 0$$




HOW TO USE KIRCHHOFF'S 2ND RULE: CONVENTION

- **Draw a circuit diagram:** Label all known and unknown quantities.
- **Assign a direction to the current:** Draw and label a current arrow I to show your choice.
- **Travel around the loop:** Choose any direction.
Resistance Rule: For a move through resistance in the direction of the current, the change in potential is $-iR$; in the opposite direction, it is $+iR$.
EMF Rule: For a move through an ideal EMF device in the direction of the EMF arrow ($-$ to $+$), the change in potential is $+\mathcal{E}$; in the opposite direction, it is $-\mathcal{E}$.
- **Apply the loop law:** $\sum(\Delta V_i) = 0$.


TESTING CONCEPTS (1): SINGLE LOOP CIRCUITS

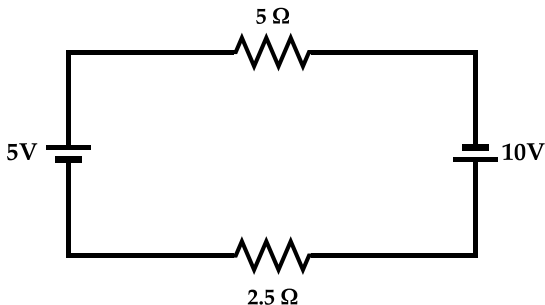Q: Find the current and potential differences across each resistor.




TESTING CONCEPTS (2): SINGLE LOOP CIRCUITS

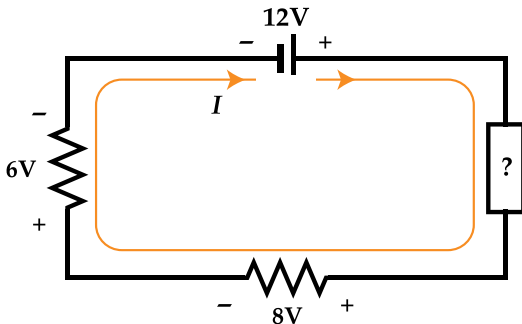Q: What is ΔV across the unspecified circuit element? Does the potential increase or decrease when traveling through this element in the direction assigned to I ?




TESTING CONCEPTS (3)

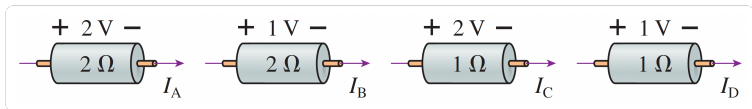Q: Rank in order, from largest to smallest, the currents I_A to I_D through the four resistors.



TESTING CONCEPTS (4): MULTI LOOP CIRCUITS

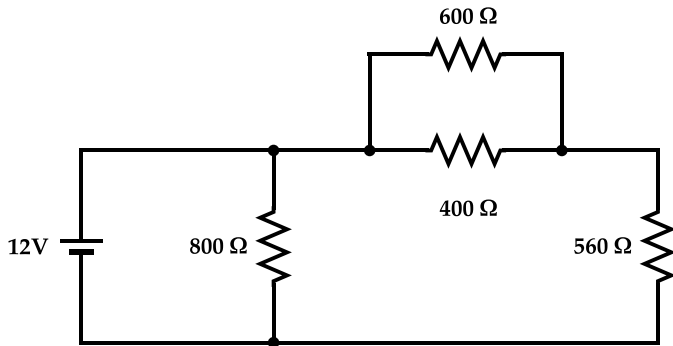Q: Find the current through and the potential difference across each of the four resistors in the circuit.



Energy Dissipation in Resistors:

$$E_{\text{chemical}} \rightarrow U \rightarrow K \rightarrow E_{\text{thermal}}$$

The battery's chemical energy is transferred to the thermal energy of the resistors, raising their temperature.

Energy exchanged per unit time is **Power**.

Power delivered by the EMF:

$$P_{\text{battery}} = \frac{\Delta U}{\Delta t} = \frac{\Delta q}{\Delta t} \mathcal{E} = I\mathcal{E}.$$

It is measured in J s^{-1} , or commonly, W.

For example, a 120 V battery that generates 2 A of current is delivering 240 W of power to the circuit.

Power dissipation through Resistors:


$$P_R = \frac{\Delta U}{\Delta t} = \frac{\Delta q}{\Delta t} V_R = I \Delta V_R = I^2 R = \frac{(\Delta V)^2}{R}.$$

It is also measured in J s^{-1} , or commonly, W.

Electric Bills are measured in terms of Kilowatt hours (kW h).

TESTING CONCEPTS (5)

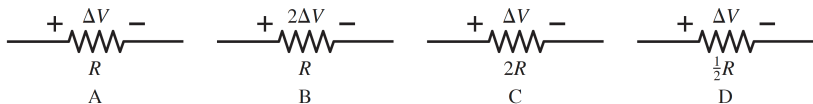Q: Rank in order, from largest to smallest, the powers P_A to P_D dissipated in resistors A to D .



TESTING CONCEPTS (6)

Q: A $6\ \Omega$ flashlight bulb is powered by a 3 V battery with an internal resistance of $1\ \Omega$. What are the power dissipation of the bulb and the terminal voltage of the battery?

Electric Bills are measured in terms of Kilowatt hours (kW h).

$$E_{\text{thermal}} = P_R \Delta t.$$

With great power comes massive electricity bills!