

PHY-112


PRINCIPLES OF PHYSICS-II

AKIFUL ISLAM (AZW)

SPRING-24 | CLASS-13

COMBINATIONS OF CAPACITORS: SERIES

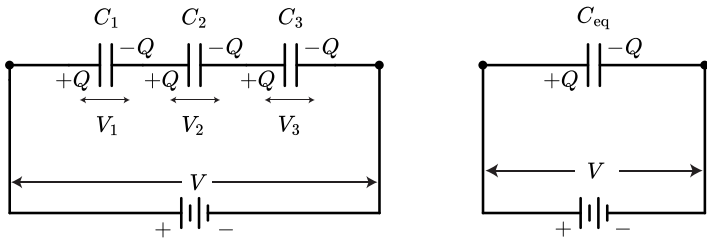
The voltage across each capacitor **is not** the same. The total voltage across the series combination equals the sum of the voltages across each capacitor.



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \sum_i^n \frac{1}{C_i}$$

COMBINATIONS OF CAPACITORS: PARALLEL

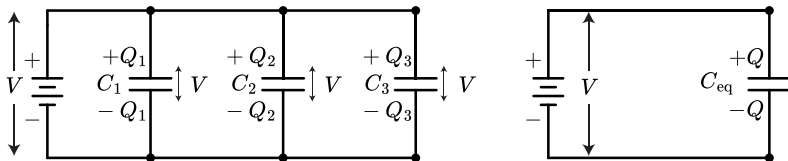
The voltage across each capacitor **is** the same. The total charge stored in the combination is the sum of the charges stored in each individual capacitor.



$$C_{eq} = C_1 + C_2 + C_3 = \sum_i^n C_i$$


TESTING CONCEPTS (1)

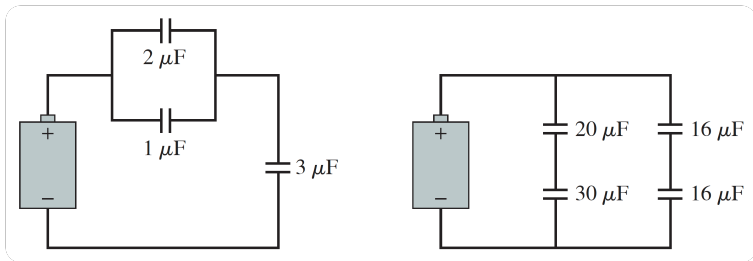Q: What is the equivalent capacitance of the following two circuits?




TESTING CONCEPTS (2)

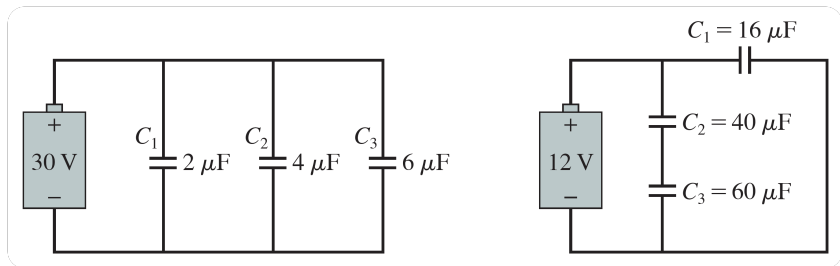Q: What are the charges and potential differences across each capacitor?




DIELECTRICS IN CAPACITOR

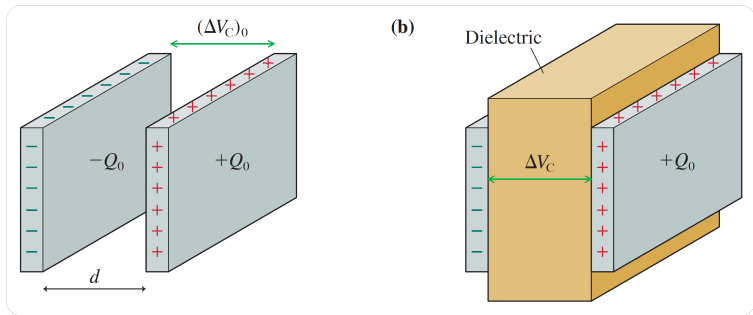Vacuum-insulated and Dielectric filled Capacitors



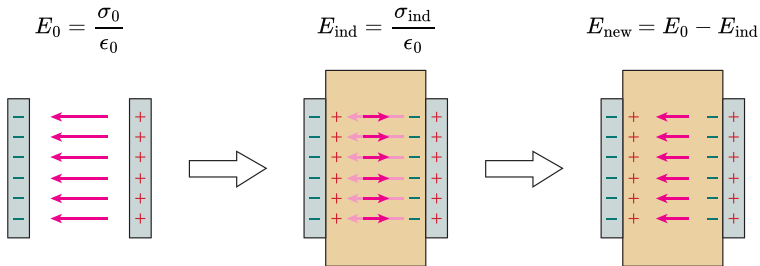THE CONSEQUENCES OF FILLING A CAPACITOR WITH A DIELECTRIC



THE CONSEQUENCES OF FILLING A CAPACITOR WITH A DIELECTRIC

Define the Dielectric Constant

$$\kappa = \frac{E_0}{E_{\text{new}}}$$

WHAT HAPPENS TO THE POTENTIAL DIFFERENCE?

$$\begin{aligned}(\Delta V_C)_{\text{new}} &= E_{\text{new}}d \\ &= \frac{E_0 d}{\kappa} \\ (\Delta V_C)_{\text{new}} &= \frac{(\Delta V_C)_0}{\kappa}\end{aligned}$$

The presence of a dielectric reduces the capacitor voltage.

WHAT HAPPENS TO THE CAPACITANCE?

$$\begin{aligned}C_{\text{new}} &= \frac{Q}{(\Delta V_C)_{\text{new}}} \\&= \frac{Q}{\left(\frac{(\Delta V_C)_0}{\kappa}\right)} \\&= \kappa \frac{Q}{(\Delta V_C)_0} \\&= \kappa C_0\end{aligned}$$

The presence of a dielectric increases the capacitance by a factor equal to the dielectric constant.

THE PERMITTIVITY OF FREE SPACE

$$\kappa = \frac{C_{\text{new}}}{C_0} = \frac{\frac{\epsilon A}{d}}{\frac{\epsilon_0 A}{d}}$$

$$\kappa = \frac{\epsilon}{\epsilon_0} = \frac{E_0}{E_{\text{new}}}$$

$$\epsilon = \kappa \epsilon_0$$

A NEW SET OF CAPACITOR EQUATIONS

$$\text{Capacitance, } C = \frac{\epsilon A}{d} = \frac{(\kappa\epsilon_0)A}{d}.$$

$$\text{Energy Density, } u_C = \frac{1}{2}\epsilon E^2 = \frac{1}{2}(\kappa\epsilon_0)E^2.$$

TESTING CONCEPTS (3)

Q: A 5.0 nF parallel-plate capacitor is charged to 160 V . It is then disconnected from the battery and immersed in distilled water ($\kappa = 78.57$). What are—

- the capacitance and voltage of the water-filled capacitor
- the energy stored in the capacitor before and after its immersion?

TESTING CONCEPTS (4)

Q: A chest defibrillator unit contains a 150 mF capacitor that is charged to 2100 V . The capacitor plates are separated by a 0.050 mm -thick insulator with dielectric constant 120 .

- What is the area of the capacitor plates?
- What are the stored energy and the energy density in the electric field when the capacitor is charged?