

## Course: Principles of Physics II (Physics 112)

Time:20min


ID:

Name:

Sec:

(An	swer any 5 questions)	
1.	a) What is the end correction of a meter bridge?	1
	b) Suppose the values of end corrections x and y of a meter bridge are respectively 1 cm and –0.5 cm. How will you use these values in your experiment?	ll 2
2.	a) Draw a circuit with four resistances and explain the Wheatstone bridge principle.	1.5
	b) What is specific resistance? Write down the factors on which specific resistance is dependent 1	1.5
3.	a) Why do you use shunt when determining the resistance of a galvanometer? Will you prefer a low or high resistance of a shunt?	1
	b) Draw the circuit for determining resistance of a galvanometer. Explain the importance of the resistances in the circuit except shunt	ne 2
	4. a) What do you understand by the term time constant of an RC circuit?	1.5
	b) Below is a graph of capacitor voltage vs time of a RC circuit while charging. Calculate	
	the time constants of this RC circuit.	1.5
	24 8 16 10 10	

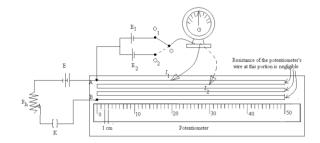b) See the figure below which shows the circuit construction to compare the emf of two cells with a potentiometer. When  $OO_1$  is connected then the null point of the galvanometer is found at  $J_1$ . When  $OO_2$  is connected then the null point of the galvanometer is found at  $J_2$ . What is the approximate of  $E_1/E_2$ ?



6. a) Draw an appropriate circuit and explain voltage divider rule.

1

- b) We can use a voltmeter/multi-meter and a resistance box to measure the internal resistance of a cell. What might be a drawback of using a voltmeter or a multi-meter for this purpose? How can a potentiometer be useful to avoid this drawback?
- 7. a) What is the mechanical equivalent of heat?

1

b) Why is it important to make radiation correction in determining mechanical equivalent of heat?

2

8. a) What is the time base of an oscilloscope?

1

b) What is Lissajous curve? From the below Lissajous curve determine  $T_x/T_y$ ?

2

